

“**Potential**” refers to a value at a single point. Across a circuit component, current will flow from a point with higher potential to a point with lower potential.


“**Potential difference**” (p.d.) refers to the difference when we compare the potential values across the two ends of a circuit component.

e.g. p.d. across a resistor,  $V_{AB} = V_A - V_B$

If potential  $V_A >$  potential  $V_B$ , a current flows.

If  $V_A = V_B$ ,  $V_{AB} = 0$ , no current flows.

For  $n$  resistors in series,

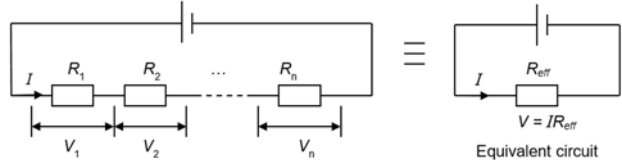


$I$  is constant (same  $I$  flowing through each resistor)

$$V = V_1 + V_2 + \dots + V_n$$

$$IR_{\text{eff}} = IR_1 + IR_2 + \dots + IR_n$$

$$R_{\text{eff}} = R_1 + R_2 + \dots + R_n$$

For  $n$  resistors in parallel,

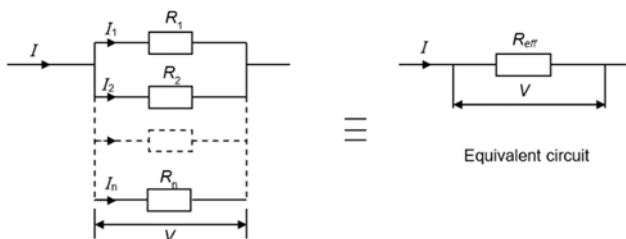

$V$  is constant (same p.d. across each resistor)

$$I = I_1 + I_2 + \dots + I_n$$

$$V/R_{\text{eff}} = V/R_1 + V/R_2 + \dots + V/R_n$$


$$1/R_{\text{eff}} = 1/R_1 + 1/R_2 + \dots + 1/R_n$$

$R_{\text{eff}}$  is always less than the value of smallest individual resistance  $R$ .

## D.C. CIRCUITS

### Potential Divider

(for resistors connected in series)

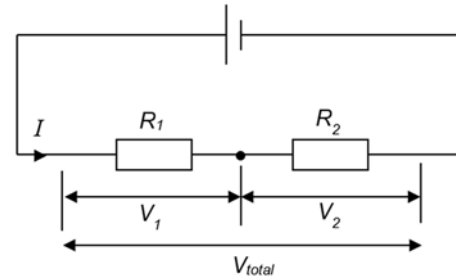

$$I = \frac{V_{\text{total}}}{R_{\text{total}}} = \frac{V_{\text{total}}}{R_1 + R_2}$$

$$V_1 = IR_1 = \frac{R_1}{R_{\text{total}}} V_{\text{total}} ; \quad V_2 = IR_2 = \frac{R_2}{R_{\text{total}}} V_{\text{total}}$$

$$\text{Ratio of p.d. across the two resistors } \frac{V_1}{V_2} = \frac{R_1}{R_2}$$

In general,


$$V_R = \frac{R}{R_{\text{total}}} V_{\text{total}} \quad \text{or} \quad \frac{V_R}{V_{\text{total}}} = \frac{R}{R_{\text{total}}}$$

### Practical uses of potential divider circuit

**Thermistor** is a semiconductor whose resistance  $R_t$  changes with temperature. Most thermistors have a *negative temperature coefficient* (NTC), meaning its resistance *decreases* as temperature *increases*.

**Light-Dependent Resistor (LDR)** is a semiconductor whose resistance *decreases* as light intensity falling on them *increases*.

### Potentiometer

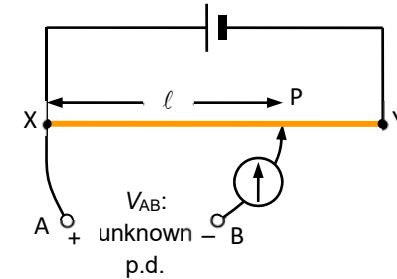


Galvanometer shows null deflection:  $V_{XP} = V_{AB}$

Applying potential divider &  $R \propto l$ ,

$$\frac{V_{XP}}{V_{XY}} = \frac{L_{XP}}{L_{XY}} \quad \text{or} \quad V_{XP} = \frac{V_{XY}}{L_{XY}} L_{XP}$$

Potentiometer is like an ideal voltmeter (which draws no current).
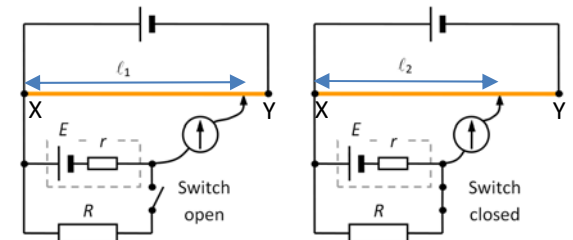
### Determining unknown internal resistance $r$



**Switch opened:** Whether or not  $E$  has  $r$  and independent of value of  $r$  (since there is no

current passing  $r$ ),  $l_1$  will not change.  $E = \frac{V_{XY}}{L_{XY}} l_1$

$$\text{Switch closed: } V_R = \frac{ER}{R+r} = \frac{V_{XY}}{L_{XY}} l_2 \Rightarrow \frac{R}{R+r} = \frac{l_2}{l_1}$$