

**Current**

Electric current is the rate of flow of charge.

$$I = \frac{dq}{dt}$$

Unit: Ampere (A)

**Charge**

Charge passing a given point is the product of current and time during which the current flows.

Total Charge is an integer multiple of the elementary charge:

$$Q = Ne$$

Unit: Coulomb (C)

One coulomb is the quantity of electric charge that pass a given point in a circuit when a steady current of 1 ampere flows through that point for 1 second.

$$I = nAvq$$

n: number density of charge carriers

v: drift velocity of charge carriers

q: charge of a charge carrier

A: cross-sectional area of conductor

**Potential Difference**

The potential difference between 2 points in a circuit is the energy converted from electrical energy to other forms of energy per unit electric charge moved between the 2 points.

$$V = \frac{W}{Q}$$

Unit: Volt (V)

One volt is the potential difference across two points in a circuit in which one joule of electrical energy is converted to other forms of energy when one coulomb of charge is moved between the two points.

**Electromotive Force (e.m.f)**

The e.m.f of a source is the energy converted from non-electrical energy per unit electric charge in driving a charge round a complete circuit.

$$E = \frac{W}{Q}$$

Unit: Volt (V)

E.m.f is about a source generating and supplying electrical energy to a circuit while P.D is a measure of the ability of a particular part of the circuit or device in the circuit to dissipate electrical energy.

**Resistance**

Ratio of the potential difference  $V$  across the device to the current flowing  $I$  across it.

$$R = \frac{V}{I}$$

Unit: Ohm ( $\Omega$ )


One ohm is the resistance of a device through which a current of one ampere flows when a potential difference of one volt exists across it.

**Resistivity**

Resistance and resistivity are related by

$$R = \rho \frac{l}{A}$$

**Internal resistance of a cell**

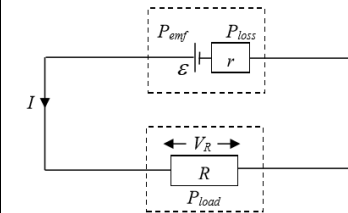

When switch is OPEN, voltmeter reads  $E$ , since no current flows and there is no potential drop across internal resistance  $r$ .

When switch is CLOSED, By principle of conservation of energy,

$$P_{cell} = P_R + P_r$$

$$I\varepsilon = IV_R + IV_r$$

$$V_R = \varepsilon - V_r = \varepsilon - Ir$$

With the switch closed, current flows in the circuit and there is a potential drop across internal resistance  $r$ . Voltmeter reads  $V_r$  which is  $E$  minus the potential drop across  $r$ . We see that the terminal pd is lower than  $E$  now.

**Power Dissipation**

$$P = IV$$


$$P = I^2R$$

$$P = \frac{V^2}{R}$$

**a) Ohmic conductor at constant temperature**


Obeys Ohm's Law.

**Metallic Conductor**

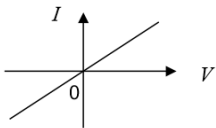

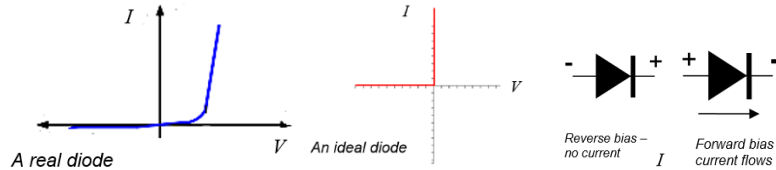**c) Diode**


Conducts well in one direction, but badly in other direction. An ideal diode has no resistance in forward-bias and infinite resistance in reverse-bias.



**b) Filament lamp**


Resistance increases with increasing temperature (when  $I$  and  $V$  are larger) due to more frequent collisions between free electrons and lattice atoms which vibrate more vigorously at higher temperatures. There is no change in number of charge carriers.

**Filament Lamp**

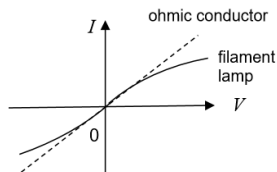


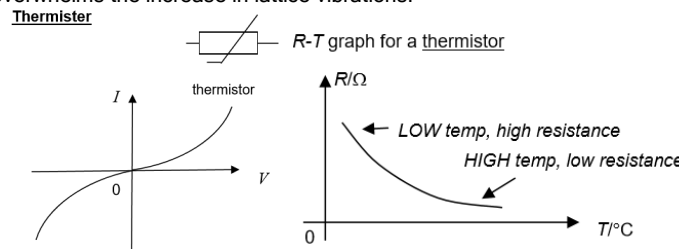**d) Negative Temperature Coefficient (NTC) Thermistor**

Resistance decreases with increasing temperature due to large increase in number of charge carriers at high temperature (it is a semiconductor material). This effect overwhelms the increase in lattice vibrations.



### Series Circuit

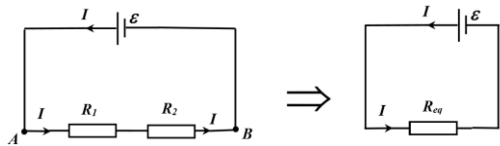

Consider 2 resistors in series (same  $I$  in both resistors).

$$V_{AB} = V_1 + V_2$$


$$IR_{equivalent} = IR_1 + IR_2$$

$$R_{equivalent} = R_1 + R_2$$

For  $n$  resistors,

$$R_{equivalent} = R_1 + R_2 + \dots + R_n$$

### Parallel Circuit

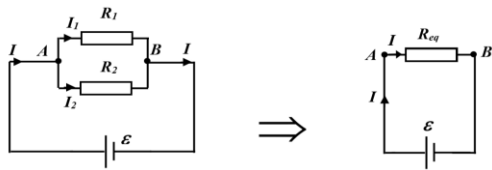

Consider 2 resistors in parallel (same  $p.d.$  across both resistors).

$$I = I_1 + I_2$$


$$\frac{V_{AB}}{R_{equivalent}} = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2}$$

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2}$$

For  $n$  resistors,

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

### Potential Divider Rule

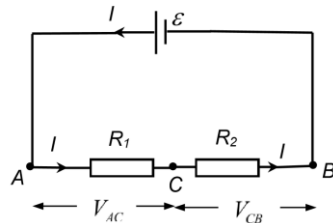

Consider 2 resistors in series (same  $I$  in both resistors).

$$V_{AC} = \frac{R_1}{R_1 + R_2} V_{AB}$$

$$V_{CB} = \frac{R_2}{R_1 + R_2} V_{AB}$$

$R_1$  or  $R_2$  can also be a...

#### 1) Thermistor

A semiconductor device whose resistance decreases as temperature increases.


The  $p.d.$  across the thermistor thus varies with temperature and the circuit can be designed to trigger fire alarms and thermostats.

#### 2) Light dependent resistor (LDR)

A semiconductor device whose resistance decreases as light intensity increases.

The  $p.d.$  across the LDR thus varies with illumination and the circuit can be designed to switch on lights when light intensity is low.

### Potentiometer

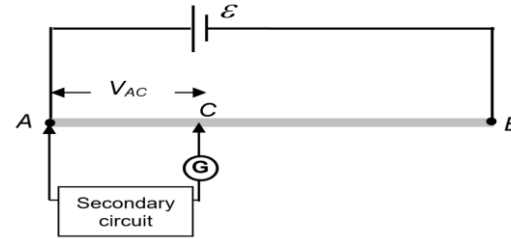


AB is a uniform length resistance wire.

Therefore,  $R \propto \text{length}$  ( $\therefore R = \rho \frac{l}{A}$ )

From potential divider rule,  $V_{AC} = \frac{R_{AC}}{R_{AB}} V_{AB} = \frac{l_{AC}}{l_{AB}} V_{AB}$

The potentiometer is like an ideal voltmeter which draws no current:
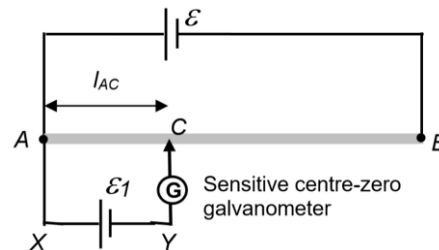
### Determine an unknown e.m.f. $\epsilon_1$ of a cell.




When galvanometer shows null deflection, no current flows in  $AX$  and  $CY$ . (note that there is still current flowing in  $ABEF$ ).

$$\epsilon_1 = V_{XY} = V_{AC} = \frac{l_{AC}}{l_{AB}} V_{AB}$$

By measuring  $l_{AC}$ ,  $l_{AB}$  and  $V_{AB}$ , the unknown  $\epsilon_1$  can be found.

Note: Whether or not  $\epsilon_1$  has internal resistance the balance length  $l_{AC}$  will not change. There is no current in  $XY$ , so there is no potential drop across the internal resistance of  $\epsilon_1$ .  $V_{AC}$  is still equal to  $\epsilon_1$ .
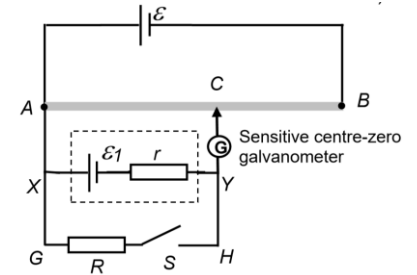
### Determine unknown internal resistance $r$ of a cell.



When galvanometer shows null deflection and switch is open, the balance length allows  $\epsilon_1$  to be found, as in case on the left.

When switch is closed and galvanometer reads null, while no current flows in  $AX$  and  $CY$ , a current flows within the lower circuit ( $X$  to  $G$  to  $H$  to  $Y$  to  $X$ ) and  $V_{XY}$  is now less than  $\epsilon_1$ .

This new  $V_{XY}$  can be found from the decreased balance length.

This  $V_{XY}$  is the terminal  $p.d.$  across the battery, which is also the potential drop or difference across  $R$ .

Thus with the switch closed,

$$V_{xy} = \epsilon_1 - Ir = \epsilon_1 - \left(\frac{V_{xy}}{R}\right)r$$

$r$  can therefore be found, since  $V_{xy}$ ,  $R$  and  $\epsilon_1$  are known.

